

VE215

Assignment #6

Fall 2016

Problem 1

Calculate $v(t)$ for $t > 0$ in the circuit of Fig. 1.

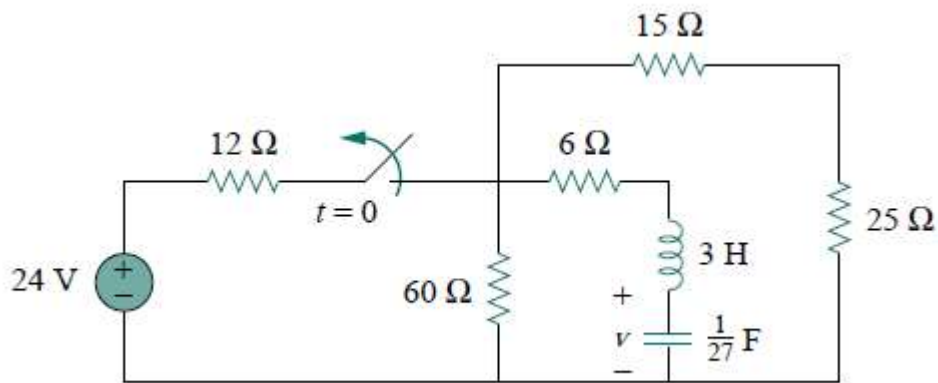


Figure 1

Problem 2

Derive the differential equation relating v_o to v_s in the op amp circuit of Fig.1.

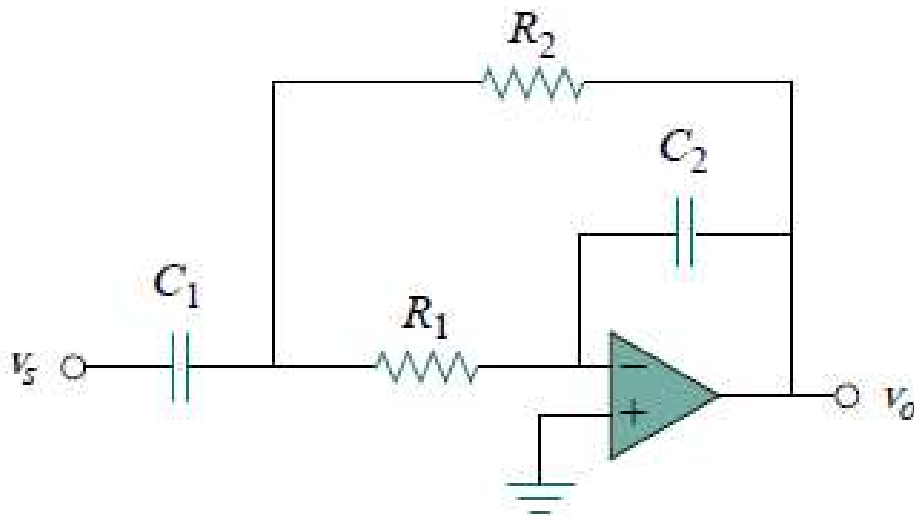


Figure 2

Problem 3

An automobile airbag igniter is modeled by the circuit in Fig. 3. Determine the time it takes the voltage across the igniter to reach its first peak after switching from A to B . Let $R = 3\ \Omega$, $C = 1/30\ \text{F}$, and $L = 60\ \text{mH}$.

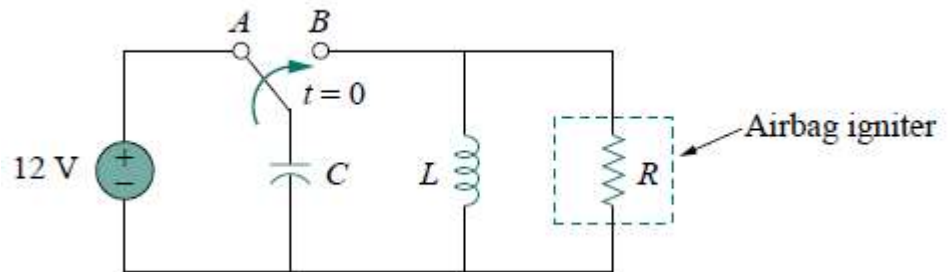


Figure 3

Problem 4

The circuit in Fig. 4 is the electrical analog of body functions used in medical schools to study convulsions. The analog is as follows:

C_1 = Volume of fluid in a drug

C_2 = Volume of blood stream in a specified region

R_1 = Resistance in the passage of the drug from the input to the blood stream

R_2 = Resistance of the excretion mechanism, such as kidney, etc.

v_0 = Initial concentration of the drug dosage

$v(t)$ = Percentage of the drug in the blood stream

Find $v(t)$ for $t > 0$ given that $C_1 = 0.5\ \mu\text{F}$, $C_2 = 5\ \mu\text{F}$, $R_1 = 5\ \text{M}\ \Omega$, $R_2 = 2.5\ \text{M}\ \Omega$, and $v_0 = 60u(t)\ \text{V}$.

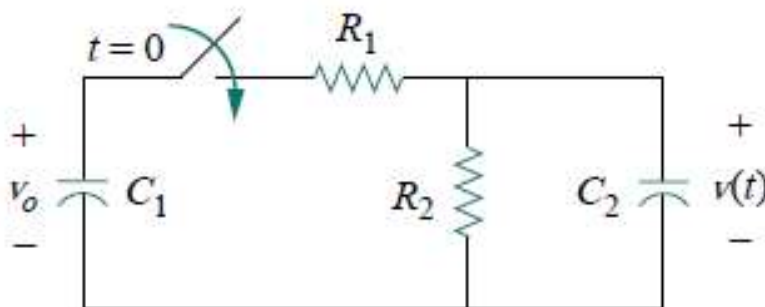


Figure 4