

VE215

Assignment #8

Fall 2016

Problem 1

In the circuit of Fig. 1, determine the average power absorbed by the 40Ω resistor.

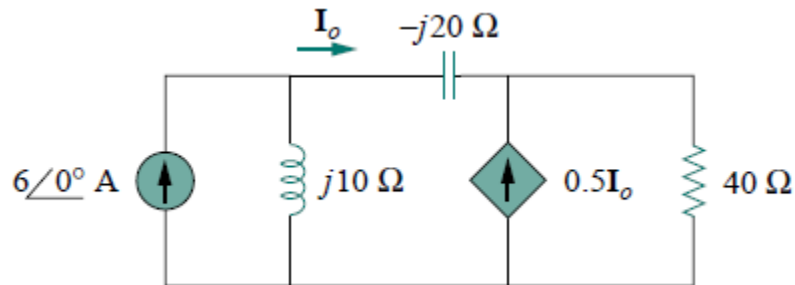


Figure 1

Problem 2

Find the value of Z_L in the circuit of Fig. 2 for maximum power transfer.

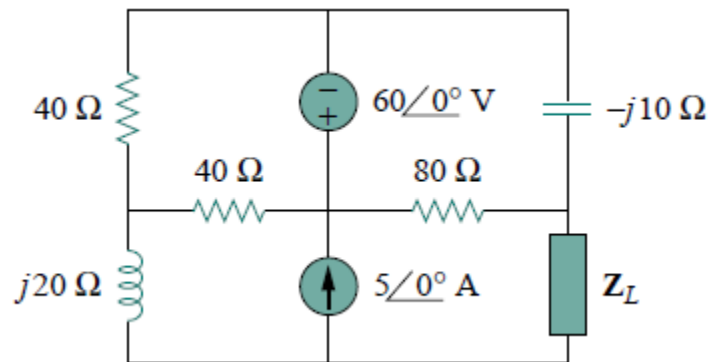


Figure 2

Problem 3

Find the rms value of the voltage waveform of Fig.3 as well as the average power absorbed by a 2Ω resistor when the voltage is applied across the resistor.

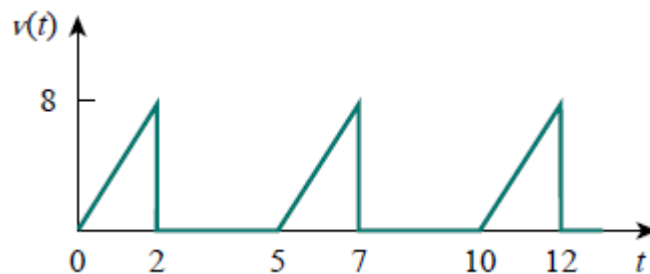


Figure 3

Problem 4

For the entire circuit in Fig. 4, calculate:

- (a) the power factor
- (b) the average power delivered by the source
- (c) the reactive power
- (d) the apparent power
- (e) the complex power

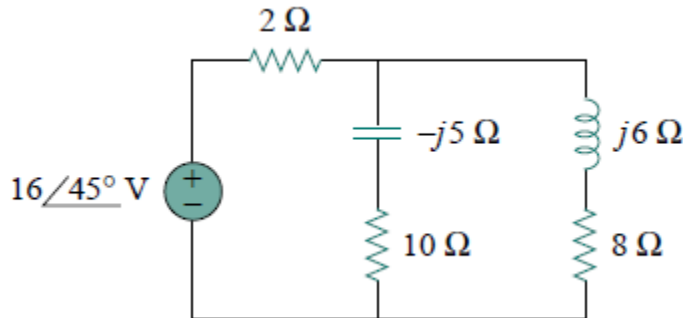


Figure 4

Problem 5

Calculate the complex power delivered to each resistor and capacitor in the op amp circuit of Fig.5. Let $v_s = 2 \cos 103t$ V.

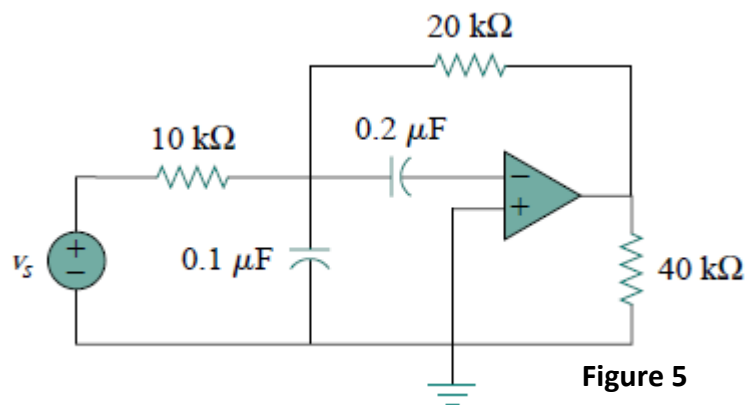


Figure 5

Problem 6

As shown in Fig. 6, a 550-V feeder line supplies an industrial plant consisting of a motor drawing 60 kW at 0.75 pf (inductive), a capacitor with a rating of 20 kVAR, and lighting drawing 20 kW.

- (a) Calculate the total reactive power and apparent power absorbed by the plant.
- (b) Determine the overall pf.
- (c) Find the current in the feeder line.

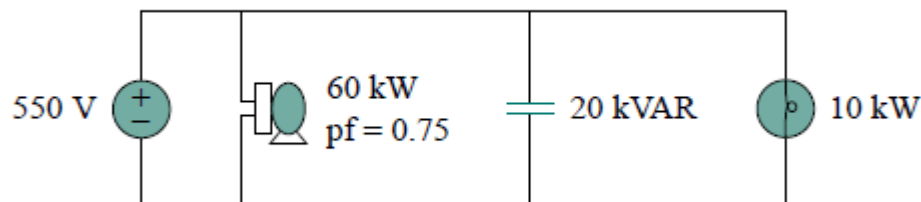


Figure 6